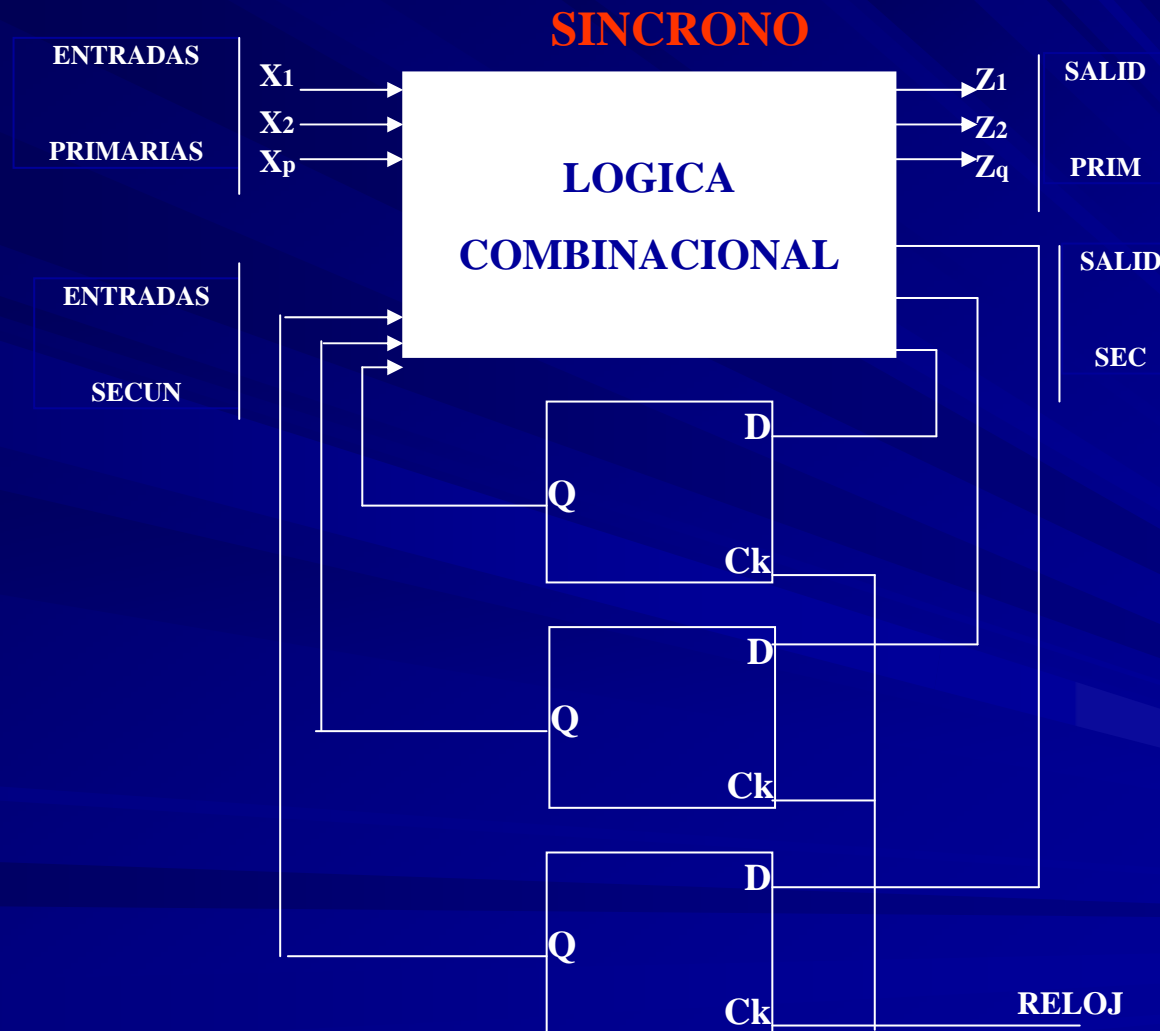




# TECNICAS DIGITALES I

## DESCRIPCION DE MAQUINAS DE ESTADOS SINCRONAS EN VHDL



# Diagrama General




# Diagrama de estados

  


# Moore y Mealy

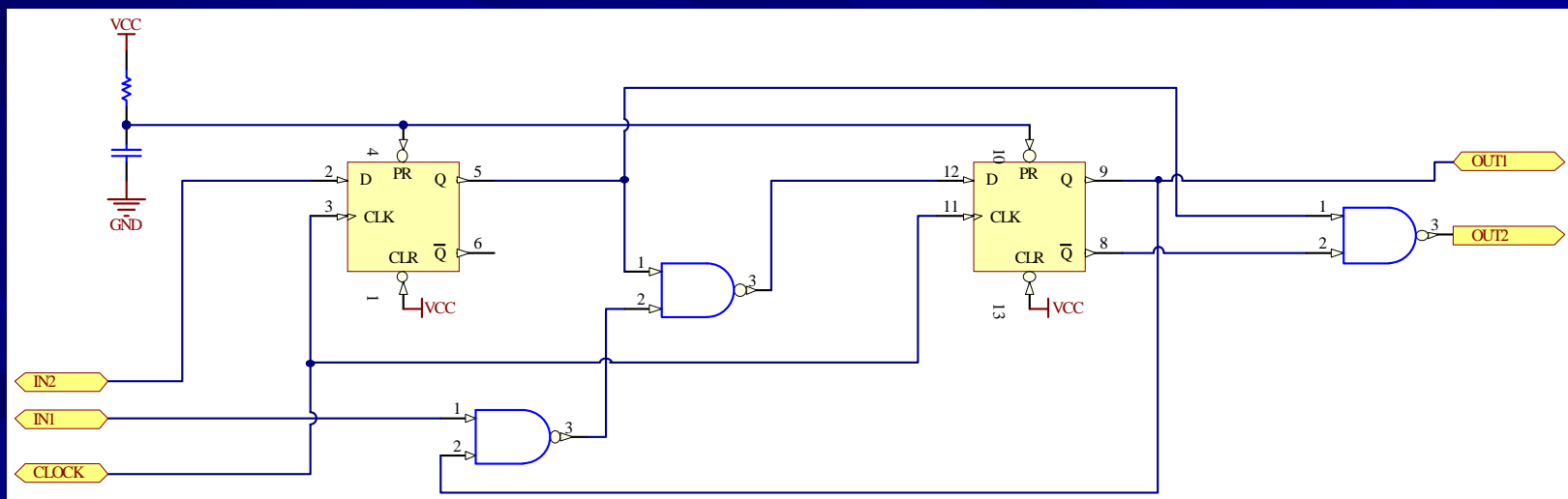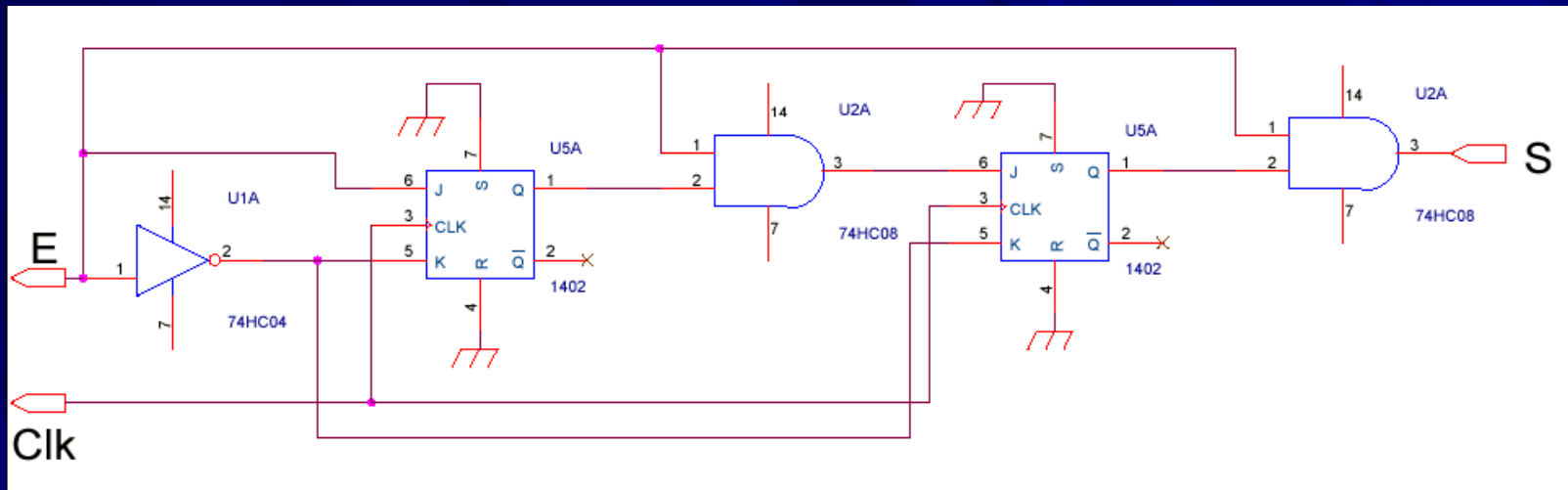


# VHDL

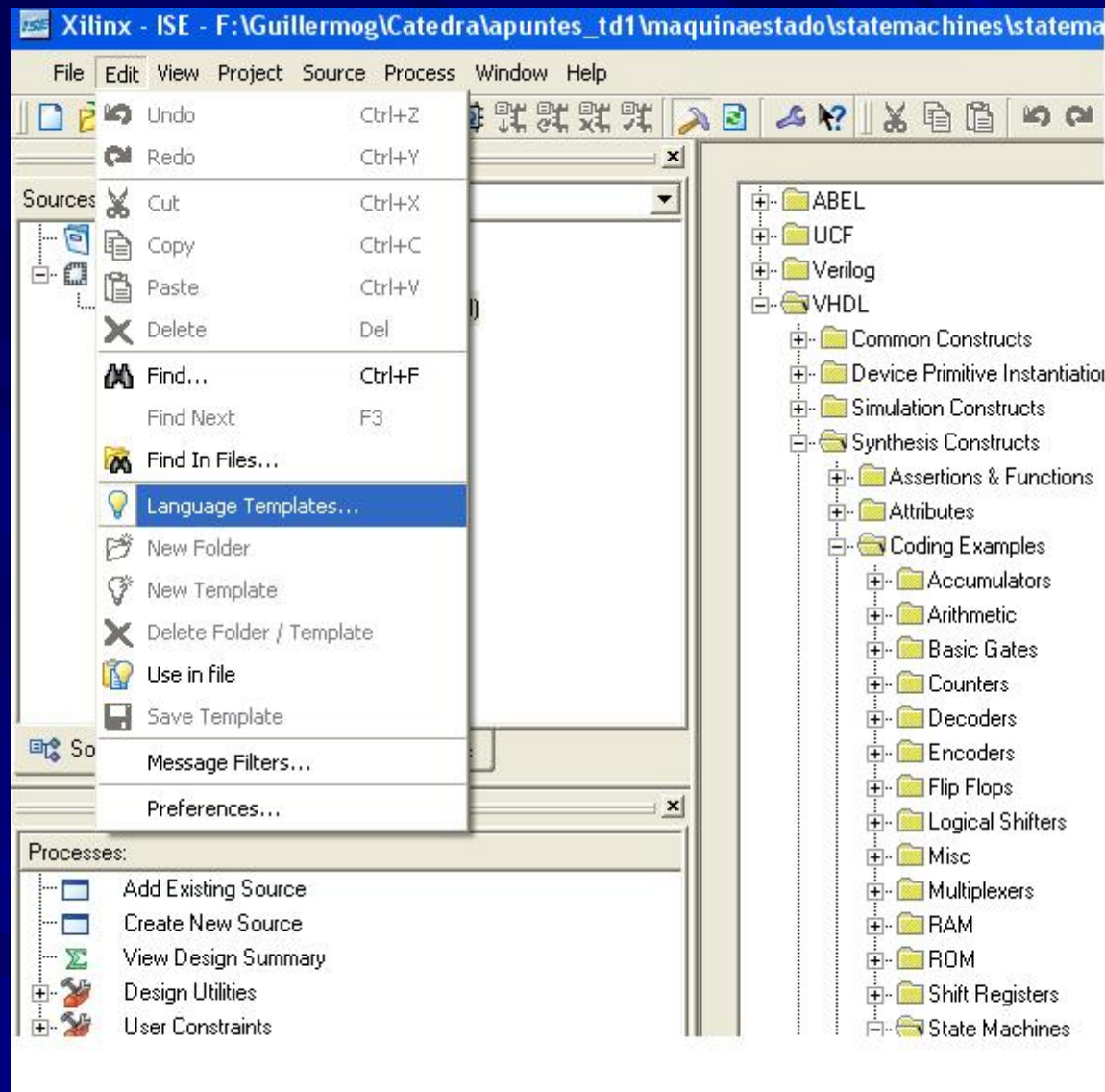

# VHDL

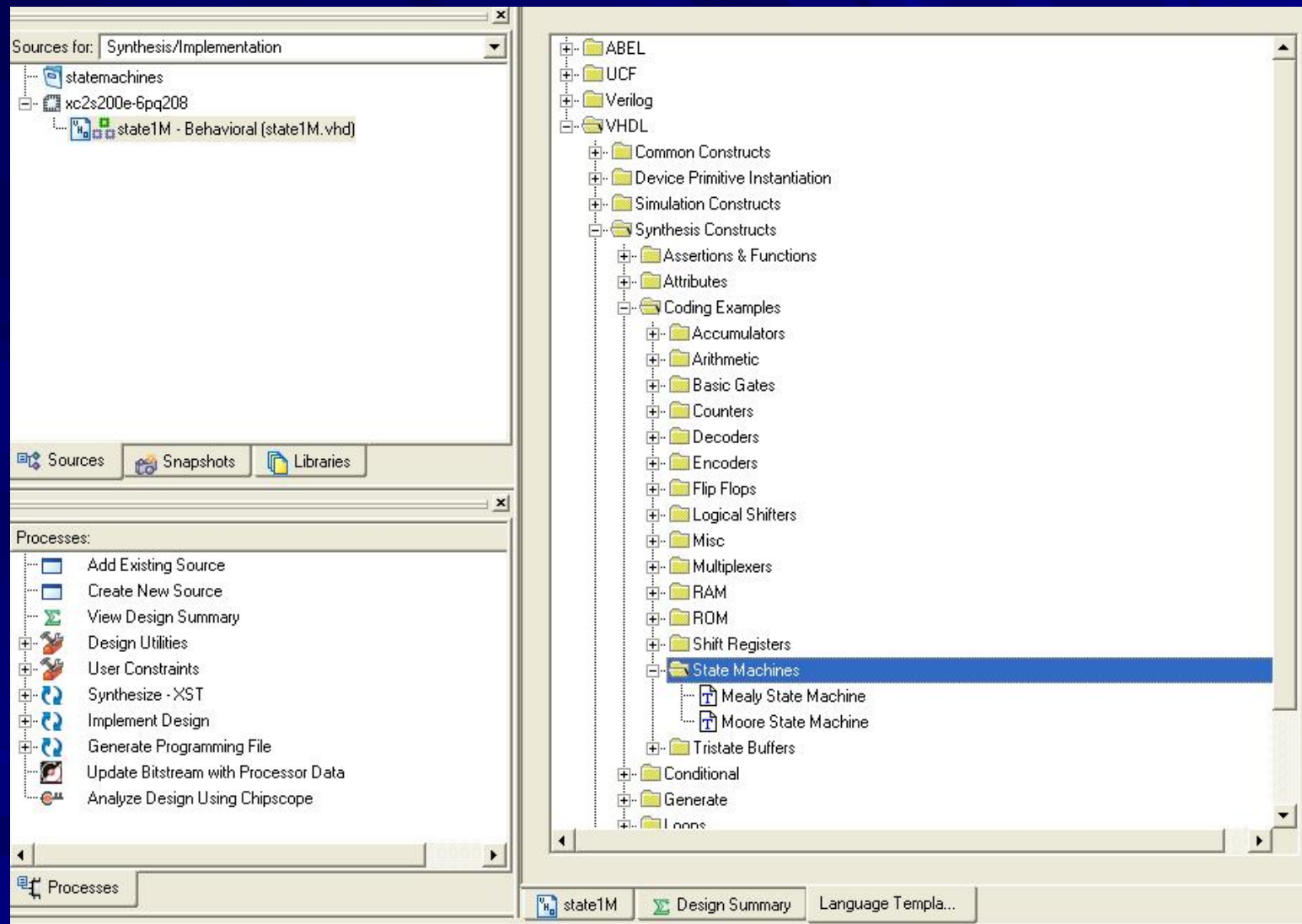

# VHDL

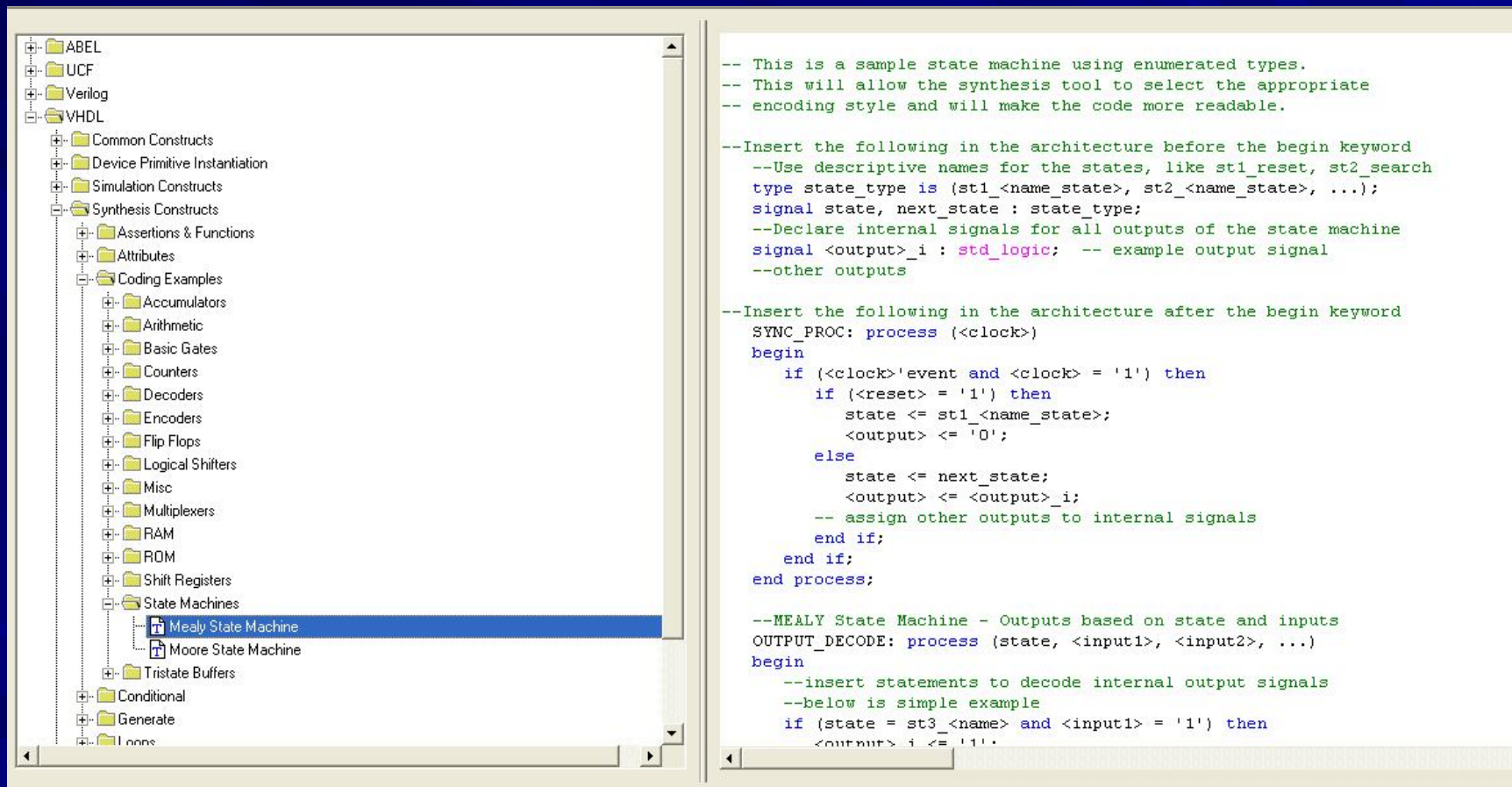

The screenshot displays a VHDL development environment. On the left is a file explorer showing a hierarchical tree of VHDL constructs. The 'VHDL' folder is expanded, revealing sub-folders like 'Common Constructs', 'Device Primitive Instantiation', 'Simulation Constructs', and 'Synthesis Constructs'. Under 'Synthesis Constructs', the 'State Machines' folder is further expanded, highlighting 'Mealy State Machine' and 'Moore State Machine'. On the right is a code editor showing VHDL code for a state machine. The code includes comments and declarations for an enumerated type, internal signals, and two processes: 'SYNC\_PROC' and 'OUTPUT\_DECODE'.

```
-- This is a sample state machine using enumerated types.
-- This will allow the synthesis tool to select the appropriate
-- encoding style and will make the code more readable.

--Insert the following in the architecture before the begin keyword
--Use descriptive names for the states, like st1_reset, st2_search
type state_type is (st1_<name_state>, st2_<name_state>, ...);
signal state, next_state : state_type;
--Declare internal signals for all outputs of the state machine
signal <output>_i : std_logic; -- example output signal
--other outputs

--Insert the following in the architecture after the begin keyword
SYNC_PROC: process (<clock>)
begin
    if (<clock>'event and <clock> = '1') then
        if (<reset> = '1') then
            state <= st1_<name_state>;
            <output> <= '0';
        else
            state <= next_state;
            <output> <= <output>_i;
            -- assign other outputs to internal signals
        end if;
    end if;
end process;

--MEALY State Machine - Outputs based on state and inputs
OUTPUT_DECODE: process (state, <input1>, <input2>, ...)
begin
    --insert statements to decode internal output signals
    --below is simple example
    if (state = st3_<name> and <input1> = '1') then
        <output>_i <= '1';
```



# Declaraciones

```
--Insert the following in the architecture before the begin keyword
--Use descriptive names for the states, like st1_reset, st2_search
type state_type is (st1_<name_state>, st2_<name_state>, ...);
signal state, next_state : state_type;
--Declare internal signals for all outputs of the state machine
signal <output>_i : std_logic; -- example output signal
--other outputs
```

## Transición de estado

```
--Insert the following in the architecture after the begin keyword
SYNC_PROC: process (<clock>)
begin
    if (<clock>'event and <clock> = '1') then
        if (<reset> = '1') then
            state <= st1_<name_state>;
            <output> <= '0';
        else
            state <= next_state;
            <output> <= <output>_i;
            -- assign other outputs to internal signals
        end if;
    end if;
end process;
```



# Lógica de salida

```
--MEALY State Machine - Outputs based on state and inputs
OUTPUT_DECODE: process (state, <input1>, <input2>, ...)
begin
    --insert statements to decode internal output signals
    --below is simple example
    if (state = st3_<name> and <input1> = '1') then
        <output>_i <= '1';
    else
        <output>_i <= '0';
    end if;
end process;
```

```
--MOORE State Machine - Outputs based on state only
OUTPUT_DECODE: process (state)
begin
    --insert statements to decode internal output signals
    --below is simple example
    if state = st3_<name> then
        <output>_i <= '1';
    else
        <output>_i <= '0';
    end if;
end process;
```

# Lógica de transición

```
NEXT_STATE_DECODE: process (state, <input1>, <input2>, ...)
begin
    --declare default state for next_state to avoid latches
    next_state <= state;  --default is to stay in current state
    --insert statements to decode next_state
    --below is a simple example
    case (state) is
        when st1_<name> =>
            if <input_1> = '1' then
                next_state <= st2_<name>;
            end if;
        when st2_<name> =>
            if <input_2> = '1' then
                next_state <= st3_<name>;
            end if;
        when st3_<name> =>
            next_state <= st1_<name>;
        when others =>
            next_state <= st1_<name>;
    end case;
end process;
```